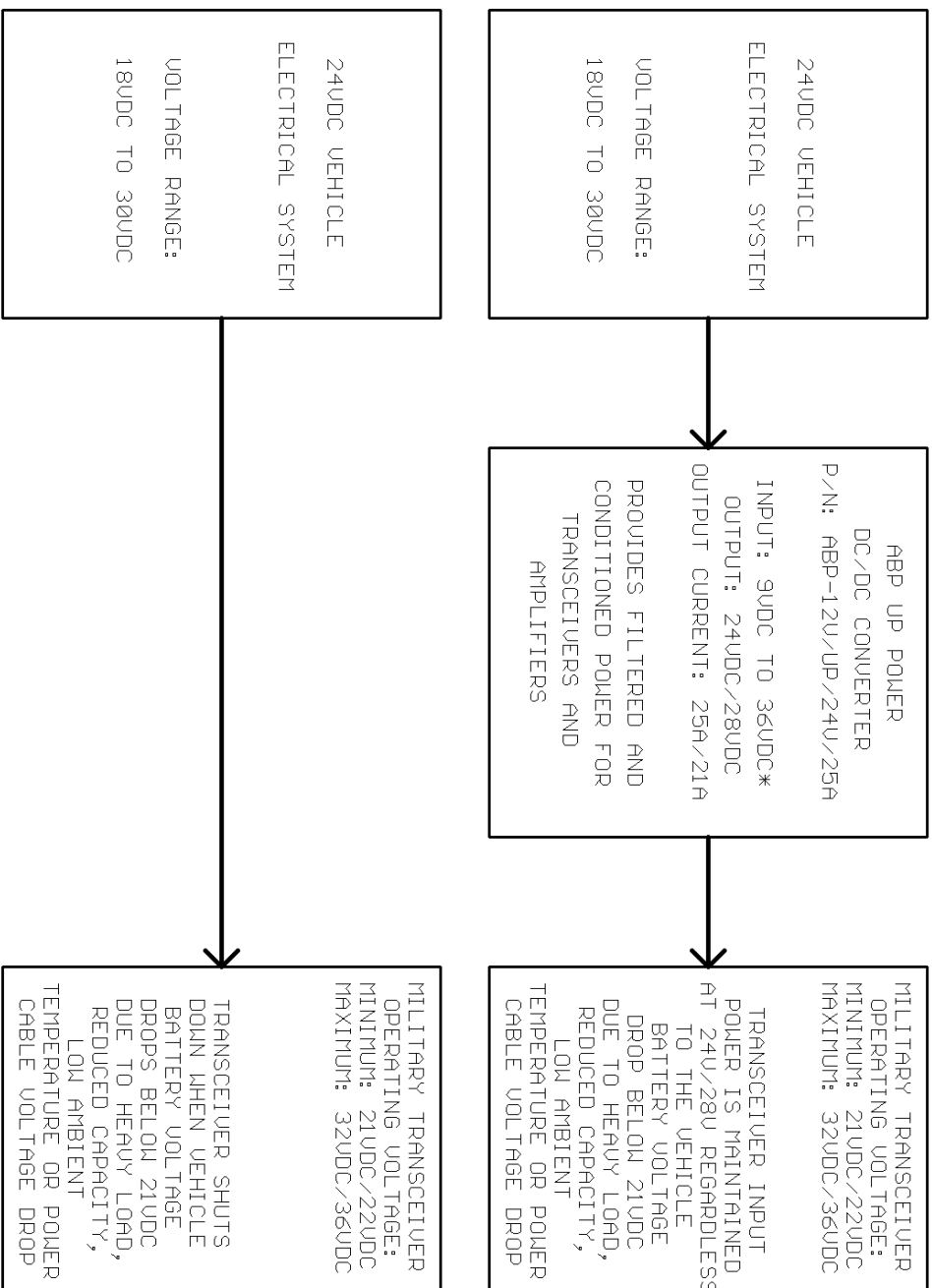


PROBLEM: TRANSCEIVER SHUTS DOWN WHEN VEHICLE BATTERY VOLTAGE IS BELOW 21VDC.

SOLUTION: INSTALL AN ABB'S UP POWER DC/DC CONVERTER BETWEEN THE VEHICLE BATTERY AND THE TRANSCEIVER.



PROBLEM

SOLUTION

* The input voltage must be lower than the output voltage.

AUTOMATED BUSINESS POWER (ABP)	
Rockville, MD (301) 424-1760	
TITLE: 24VEHCL TRANSCEIVER/AMPLIFIER OPERATION FROM A 24VDC VEHICLE ELECTRICAL SYSTEM	
Document Number:	040-0105
REU:	A
Date: 3/15/1999 06:08:02p	Sheet: 1/1